




به نام خدا



University of Tehran
Electronic and Computer Engineering
Digital Systems 1
Computer Assignment 6

Amirhossein Yavarikhoo	نام و نام خانوادگی
810199514	شماره دانشجویی
1401/3/23	تاریخ ارسال گزارش

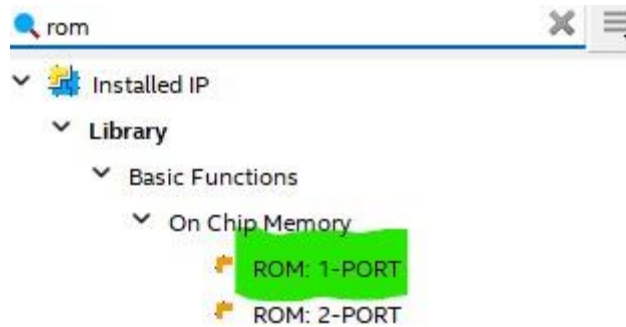To create a ROM, we use on chip memory 1-port ROM from basic function in quartus library.




To instantiate it we call it LUT(look up table).

Each word/data that is saved on this memory is a 16 bit number so the width of each word is 16 bits and the memory should have 16 words. This results in address for each memory be 4 bits (address [3:0]). Since this memory is read-only, we have to store initial values manually. To do so, first we open a new memory initialization file(.mif) from quartus. The values for $1/k$ is less than one so we have to shift them to the left by 16 bits (which equals to multiplying them by 2^{16}) and in the end consider this 16 bits as fractions.


Addr	+0	+1	+2	+3	+4	+5	+6	+7	ASCII
0	FFFF	FFFF	8000	5555	4000	3333	2AAA	2492	-----
8	2000	1C71	1999	1745	1555	1381	1249	0000	-----

Hexadecimal values for each $1/k$ is represented above.

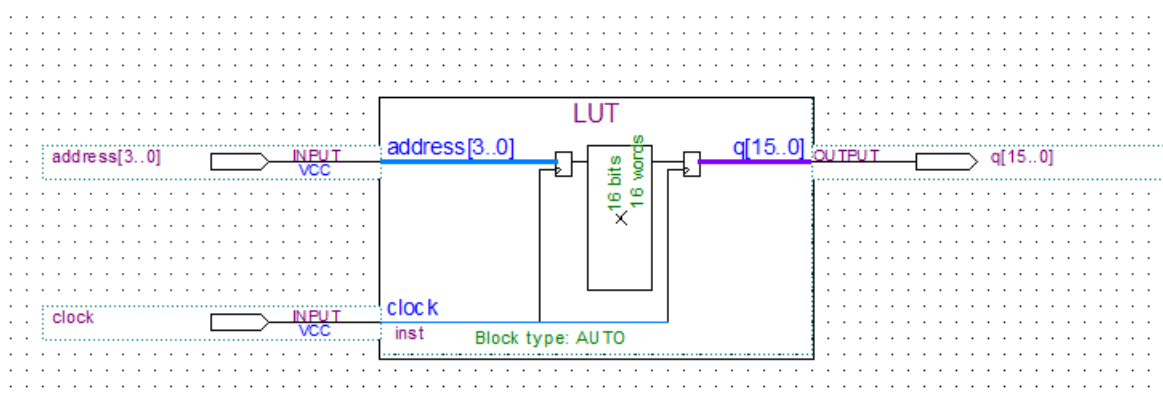We load this file in ROM and we have the look up table needed for this project.




Part B

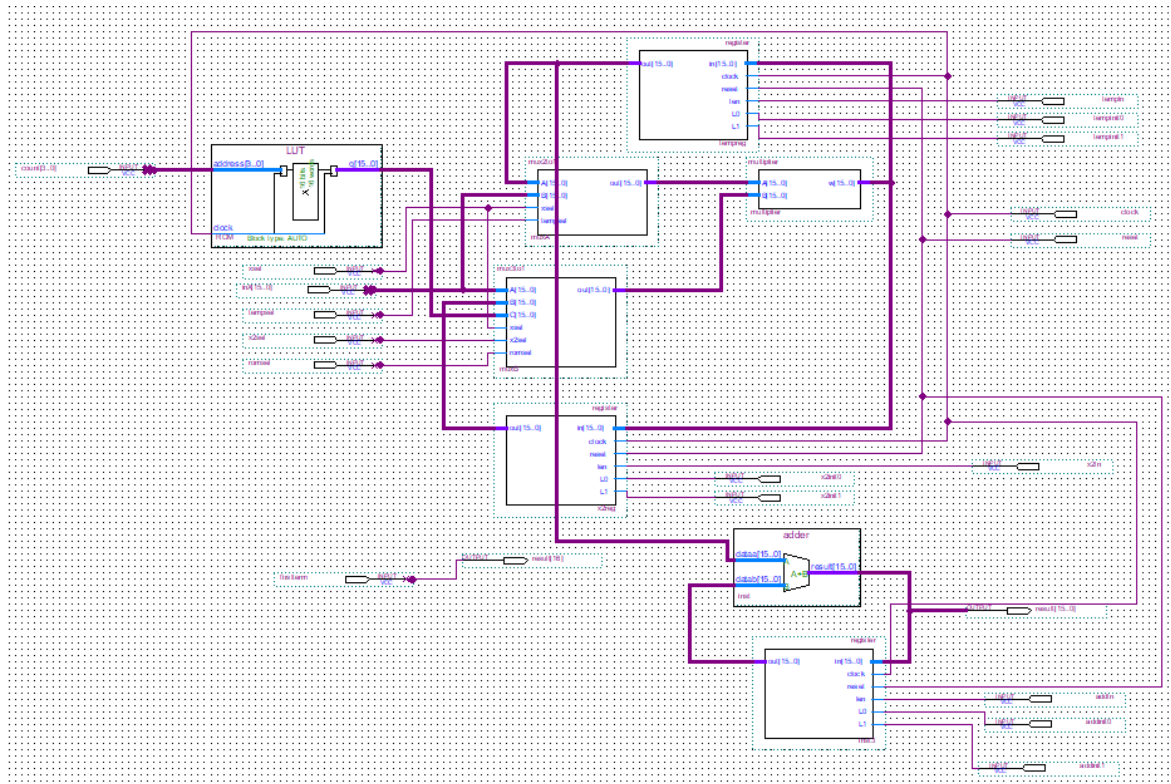

Synthesis report is shown below:

Flow Status	Successful - Tue Jun 21 17:19:20 2022
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	coshcal
Top-level Entity Name	coshcal
Family	Cyclone IV E
Total logic elements	116 / 6,272 (2 %)
Total registers	48
Total pins	53 / 92 (58 %)
Total virtual pins	0
Total memory bits	256 / 276,480 (< 1 %)
Embedded Multiplier 9-bit elements	2 / 30 (7 %)
Total PLLs	0 / 2 (0 %)
Device	EP4CE6E22C6
Timing Models	Final

State diagram:

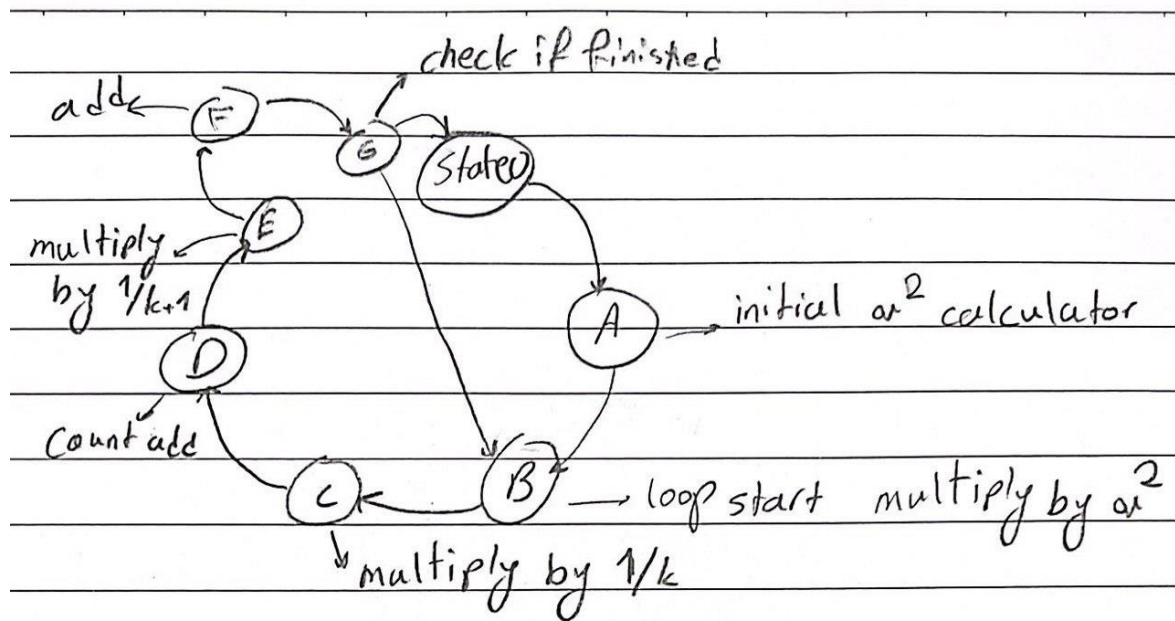

Verilog code for this state diagram is shown below:


```

1  `timescale 1ns/1ns
2  module controller (input start, clock, output reg [3:0] count, output reg xsel, tempse1,
3                      x2sel, romsel, x2init0, x2init1, x2ln, temp1n, tempinit0, tempinit1, reset, addinit0, addinit1, addin, busy, ready, output firstterm);
4      assign firstterm=1'b1;
5      reg [2:0] pstate, nstate;
6      parameter [2:0] state0=3'd0, stateA=3'd1, stateB=3'd2, stateC=3'd3, stateD=3'd4, stateE=3'd5, stateF=3'd6, stateG=3'd7;
7      assign pstate=state0;
8      always @(pstate, start) begin
9          case (pstate)
10             state0: begin
11                 reset=1;
12                 count=4'd0;
13                 ready=1;
14                 count=0; x2init0=0; x2init1=0; addinit0=0; addinit1=0; busy=0;
15                 if (start==1'b1) nstate<=stateA;
16                 else nstate<=state0;
17             end
18             stateA: begin
19                 reset=0; xsel=1; x2sel=0; romsel=0; temp1n=0; busy=1; tempse1=0; tempinit0=0; tempinit1=1;
20                 x2ln=1; ready=0;
21                 nstate<=stateB;
22             end
23             stateB: begin
24                 tempinit1=0; xsel=0; tempse1=1; x2sel=1; romsel=0; x2ln=0; addin=0; temp1n=1;
25                 nstate<=stateC;
26             end
27             stateC: begin
28                 tempse1=1; x2sel=0; romsel=1;
29                 nstate<=stateD;
30             end
31             stateD: begin
32                 temp1n=0; count=count+1;
33                 nstate<=stateE;
34             end
35             stateE: begin
36                 tempse1=1; x2sel=0; romsel=1; temp1n=1;
37                 nstate<=stateF;
38             end
39             stateF: begin
40                 addin=1; temp1n=0;
41                 nstate<=stateG;
42             end
43             stateG: begin
44                 addin=0;
45                 if (count==15) nstate<=state0;
46                 else begin nstate<=stateB; count=count+1; end
47             end
48         endcase
49     end
50     always @(posedge clock) begin
51         pstate<=nstate;
52     end
53 endmodule
54

```

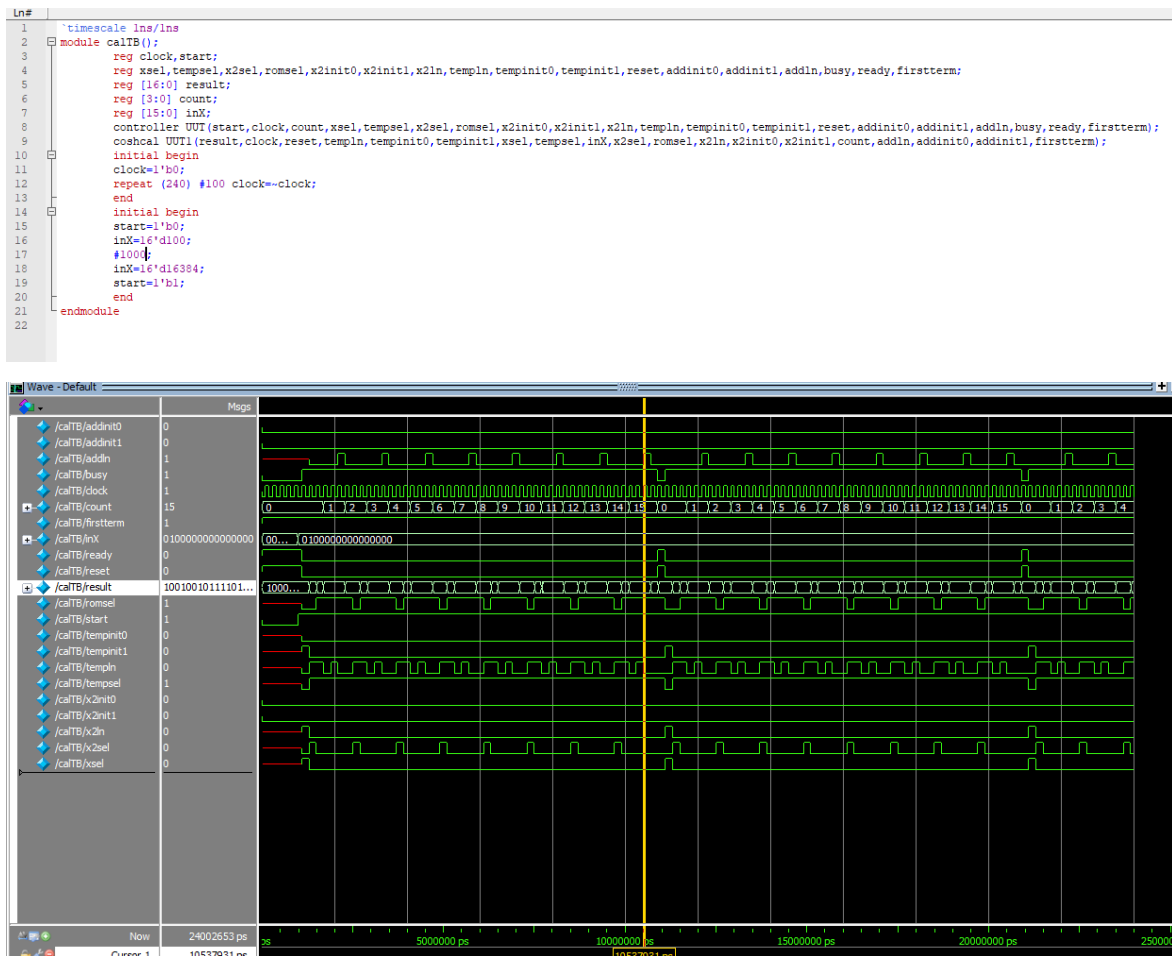Part D

Testbench for this circuit is shown below:



This value is almost the same to real cosh(0.5).

Enter binary number

1.0010010111101110 2

= Convert × Reset ↕ Swap

Decimal number

1.148162841796875 10

cosh(0.5)

1.1276259652063807852262251614027

